

國立中正大學 105 學年度碩士班招生考試試題

電磁晶片組

系所別：電機工程學系-計算機工程組

科目：電子學

晶片系統組

光機電整合工程研究所

第 2 節

第 1 頁，共 2 頁

- Consider a process technology for which $V_t = 0.6$ V, $\mu_n = 450$ cm²/Vs, $t_{ox} = 8$ nm, $L_{min} = 0.25$ μ m.
 - Find C_{ox} (4%)
 - For a MOSFET with $W/L = 5$ μ m/ 0.5 μ m, calculate the values of V_{GS} and V_{DSmin} needed to operate the transistor in the saturation region with a dc current $I_D = 80$ μ A. (6%)
 - For the device in (b), find the value of V_{GS} required to cause the device to operate as a 500- Ω resistor for very small V_{DS} . (5%)
- Design the circuit below so that the transistor operates in saturation with $I_D = 0.4$ mA and $V_D = +2$ V. Let the PMOS have $V_t = -1$ V and $k_p'(W/L) = 0.8$ mA/V². Assume $\lambda = 0$.
 - Calculate V_G , R_D , R_{G1} , and R_{G2} . (12%)
 - What is the largest value of R_D while maintaining saturation-region operation? (3%)

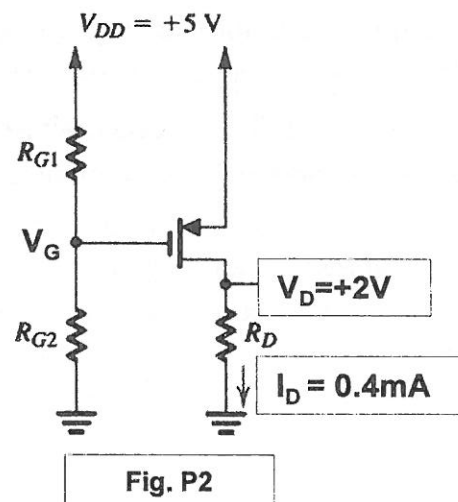


Fig. P2

- For the cascode amplifier, let Q_1 and Q_2 be identical with $V_t = 0.6$ V, $k_n' = 160$ μ A/V², $\lambda = 0.05$ V⁻¹, $\chi = g_{mb}/g_m = 0.2$, $W/L = 100$, and $V_{OV} = 0.2$ V.
 - Calculate the bias current I and the values of g_{m1} , g_{m2} , r_{o1} , r_{o2} . (6%)
 - Find the open-circuit voltage gain. (3%)
 - Calculate the value of the effective short-circuit transconductance, G_m , and the value of output impedance R_{out} of the cascode. (4%)
 - If the constant-current source I is implemented with a cascode circuit with an output resistance of 10 M Ω , find the voltage gain A_v . (4%)
 - Ignoring the small signal swing at the input and at the drain of Q_1 , find the lowest value that V_{BIAS} should have to operate Q_1 and Q_2 in saturation. (3%)

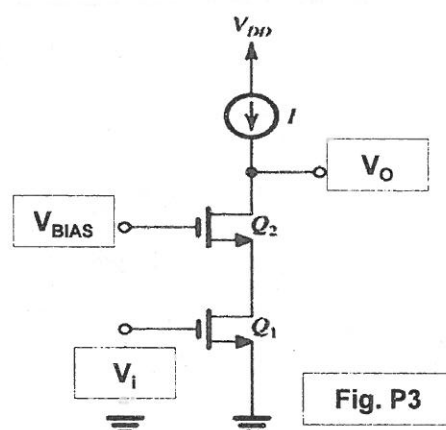


Fig. P3

4. Consider the voltage regulation circuit shown in Fig. P4, where four identical diodes in forward bias produce a total voltage of $V_O \approx 2.8$ V and a total current of $I = 8$ mA. Please compute V_O if the supply voltage (V_{IN}) becomes 3.35 V. (Note: thermal voltage $V_T = 25$ mV). (15%)

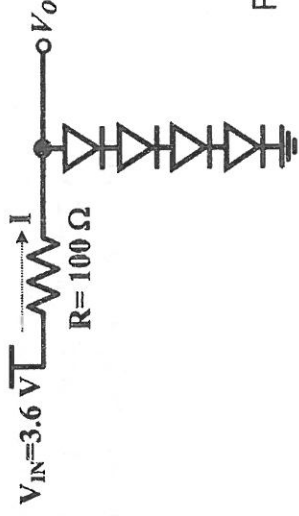


Fig. P4

5. The circuits in Fig. P5 is fabricated with the following process parameters: $\mu_n C_{ox} = 150 \mu A/V^2$, $\mu_p C_{ox} = 75 \mu A/V^2$, $V_{tn} = |V_{tp}| = 0.5$ V, and $\lambda = 0$ V⁻¹, while supply voltage (V_{DD}) is 1.8 V.
- (a) In the circuit shown in Fig. P5(a), assume $(W/L)_{Q1} = 10$, $(W/L)_{Q2} = 20$, and $V_{IN} = 1.8$ V. In case Q1 operates in the saturation region, determine the output voltage (V_{OUT}). (8%)
- (b) Considering the channel length modulation with $\lambda = 0.02$ V⁻¹ for both Q₁ and Q₂ of the circuit shown in Fig. P5(b), determine a relationship between $(W/L)_{Q1}$ and $(W/L)_{Q2}$ that set the trip point to 0.9 V with a biasing current of 120 μ A, thus providing a “symmetric” voltage transfer characteristic (VTC). In addition, determine the small-signal gain under this biasing condition. (12%)

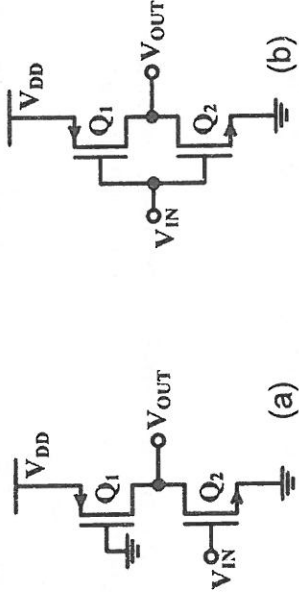


Fig. P5

6. (a) The circuit in Fig. P6(a) has $V_{i1} = 0.4$ V, $V_{i2} = 0.6$ V, $V_{i3} = 0.9$ V, and $V_{i4} = 1.1$ V, $R = 5$ K Ω , and $R_f = 1$ K Ω . Find V_o in case the operational amplifier is ideal. (3%)
- (b) An operational amplifier with an output resistance of 100 Ω was configured as the unity-gain buffer shown in Fig. P6(b) to drive a 10 Ω Load, please find the required gain (A_0) to achieve a gain error of 1% for the unity-gain buffer. (6%)

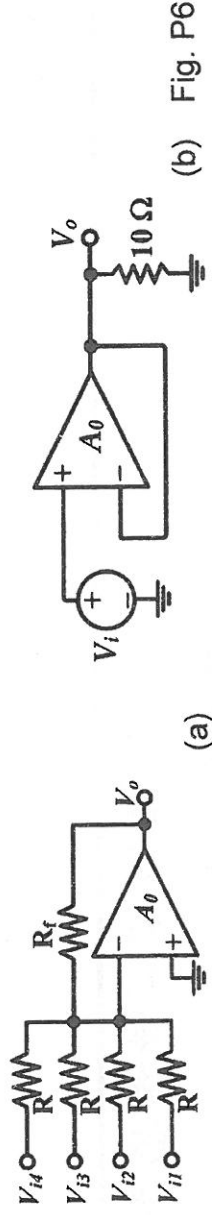


Fig. P6

7. In each of the following statements, determine whether the statement is “True” or “False”.
- a) We can increase the reverse bias voltage of a PN Junction to increase the charge stored in the depletion region. (2%)
- b) The definition of the small signal parameter r_o of a MOSFET is $\left[\frac{\partial i_D}{\partial v_{GS}} \Big|_{v_{GS}=V_{GS}} \right]^{-1}$. (2%)
- c) The increase in temperature will result in a corresponding increase in drain current of a MOSFET. (2%)