

1. (10%) Fig. P1 shows an NMOS transistor with its drain and gate terminals connected together. Find the $i-v$ relationship of the resulting two-terminal device in terms of the MOSFET parameters $k_n = k_n'(W/L)$ and V_m . Neglect channel-length modulation.

 


Fig. P1

2. (20%) Fig. P2 shows an ideal voltage amplifier having a gain of -100 V/V with an impedance Z connected between its output and input terminals. Find the Miller equivalent circuit when Z is (a) a $1\text{-M}\Omega$ resistance (b) a 1-pF capacitance. In each case, use the equivalent circuit to determine V_o/V_{sig} .

 


Fig. P2

3. (20%) Fig. P3 shows a positive-feedback circuit. (a) Find the loop transmission $L(s)$ and the characteristic equation. (b) Sketch a root-locus diagram for varying K , and find the value of K that makes the circuit oscillate.



 


Fig. P3


4. The operational amplifier (OPA) shown in Fig. P4 is an ideal OPA, and the switches $S_{i|j=1\sim N}$ are controlled by the controlling signals $b_{i|j=1\sim N}$, respectively.
- (a) Please derive the output V_o using known parameters V_{REF} , R , and $b_{i|j=1\sim N}$. (10%)
- (b) In the case of $V_{REF} = 2\text{ V}$, what the minimum bit number (N) of b_i is required to generate an output (V_o) of -1.8125 V and what is the corresponding $b_{i|j=1\sim N}$. (5%)

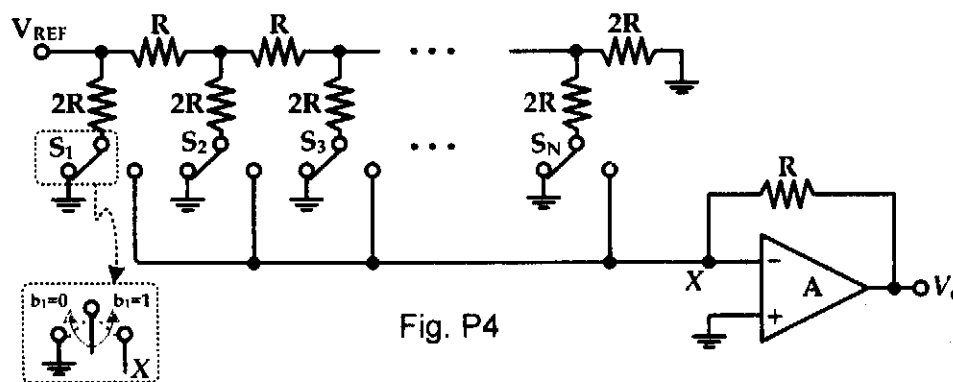

 5. Consider the voltage regulation circuit shown in Fig. P5 for the case of $V_{in} = 10\text{ V}$. Assume the diode D_1 to have a 0.7-V drop at 5 mA current while D_2 is a 6.8-V zener diode with a 6.8-V drop at 5 mA current, and an incremental resistance of $20\ \Omega$. (Note: thermal voltage $V_T = 25\text{ mV}$)
- (a) Determine the line regulation ($\Delta V_o / \Delta V_{in}$). (6%)
- (b) Determine the load regulation ($\Delta V_o / \Delta I_L$). (6%)



6. (a) Please sketch the input/output characteristic of a logic inverter, also explain the concepts of noise margin using the input/output characteristic. (5%)
- (b) Fig. P6 shows an inverter circuit, please find the output high level (V_{OH}) and output low level (V_{OL}). Assume that PMOS transistor Q has the (W/L) ratio of 100 , $\mu_p C_{OX} = 50\ \mu\text{A/V}^2$, $\lambda_p = 0\text{ V}^{-1}$, and $|V_{tp}| = 0.8\text{ V}$. (10%)

 

7. Design a row decoder for an $8\text{ words} \times 8\text{-bit}$ SRAM, please show the circuit in transistor level. (8%)