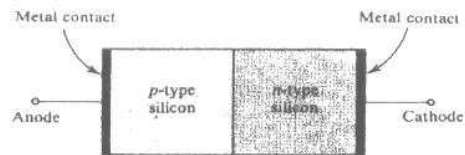


1. For the  $pn$  junction diode shown below, assuming that the  $p$  region is more heavily doped than the  $n$  region;

(a) When the  $pn$  junction is forward-biased, plot the minority-carrier distribution and the majority-carrier diffusion current density. (5%)

(b) When the  $pn$  junction is reverse-biased, plot the minority-carrier distribution and the majority-carrier diffusion current density. (5%)



2. (a) Explain "Ebers-Moll Model" for the BJT. Please draw the model. (3%)


(b) Explain what "Saturation" means in BJT's operation. (2%)

(c) Plot the high-frequency hybrid- $\pi$  model of an npn BJT transistor. Label every component. (3%)

3. Consider a design of the cascode op amp shown below for which  $I = 125 \mu\text{A}$  and  $I_B = 150 \mu\text{A}$ . Assume that all transistors are operated at  $|V_{ov}| = 0.15\text{V}$  and that for all devices, the Early voltage  $|V_A| = 12\text{V}$ .  $V_{DD} = V_{SS} = 3\text{V}$ . (20%)

(a) Calculate the overall transconductance  $G_m$ , output resistance  $R_o$ , and  $A_v = v_o/(v_i^+ - v_i^-)$ .

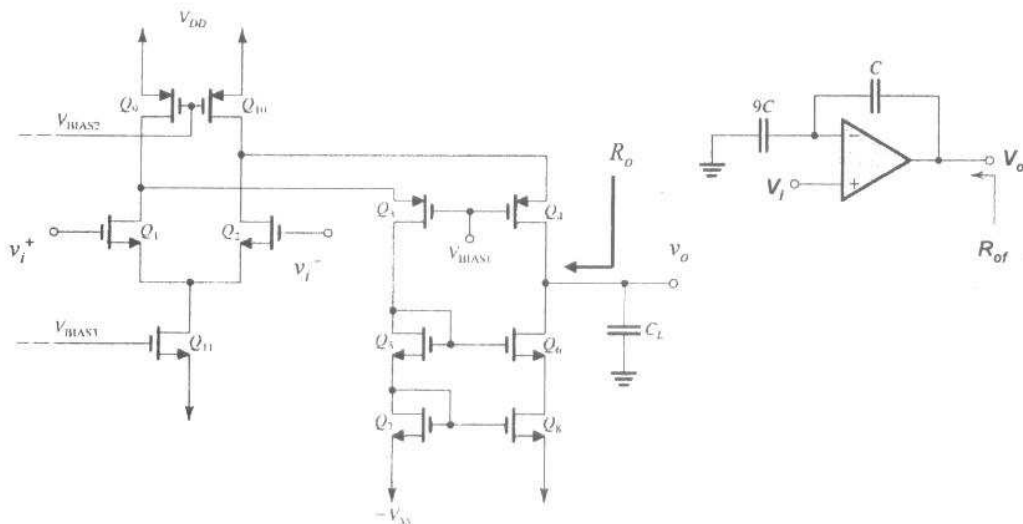
(b) If the op amp is connected in the feedback configuration shown below, find the voltage gain and the output resistance of the closed-loop amplifier.



4. Use CMOS logic circuit to realize a three-input even-parity checker. Specifically, the output  $Y$  is to be low when an even number of the inputs  $A$ ,  $B$ , and  $C$  are high. Please sketch your design. (12%)

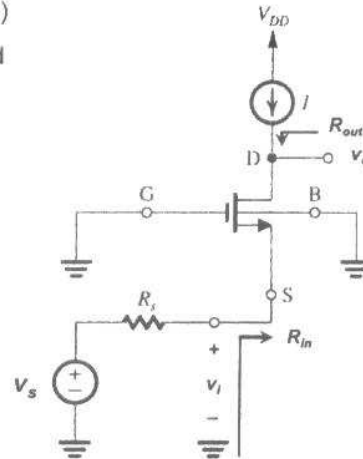
5. For the NMOS amplifier shown, (20%)

- sketch the equivalent circuit for small signal analysis, and derive the expressions for
- the input resistance  $R_{in}$ ,
- the voltage gains  $v_o/v_s$ ,
- the output resistance  $R_{out}$  and
- the 3-dB frequency  $f_H$ .



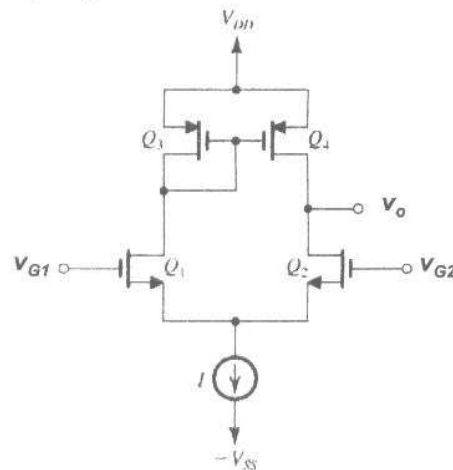6. For the active-loaded MOS differential pair, (15%)

- the output resistance  $R_o$ ,
- the differential gain  $A_d$ ,
- the common-mode gain  $A_{cm}$ , and
- the common-mode-rejection-ratio (CMRR).



7. For the feedback amplifier, the op amp is characterized by an open-loop voltage gain  $\mu$ . (15%)

- Determine the feedback type of the amplifier, and derive the expressions for
- the gain-with-feedback  $A_f \equiv i_o/v_s$ ,
- the input resistance  $R_{in}$ , and
- the output resistance  $R_{out}$ .

