

國立中正大學九十四學年度碩士班招生考試試題


系所別：光機電整合工程研究所

科目：電子學

第 2 節

第 1 頁，共 3 頁

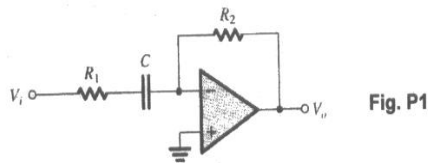1. For the circuit in Fig. P1: (12%)
  - (a) Derive the transfer function. What is the "function" of this circuit?
  - (b) Derive the expression for the high-frequency gain and the 3-dB frequency.
  - (c) Design the circuit to obtain a high-frequency input resistance of  $10\text{ k}\Omega$ , a high-frequency gain of 40 dB, and a 3-dB frequency of 1000 Hz.
  - (d) At what frequency does the magnitude of the transfer function reduce to unity?



2. For a common-emitter amplifier in Fig. P2, neglect  $r_x$  and  $r_o$ , and assume the current source to be ideal. (20%)
  - (a) Derive the expression for the midband gain.
  - (b) Derive the expression for the break frequencies cause by  $C_E$  and  $C_C$ , respectively.
  - (c) Give an expression for the amplifier voltage gain  $A(s)$ .
  - (d) For  $R_{sig} = R_C = R_L = 10\text{ k}\Omega$ ,  $\beta = 100$ , and  $I = 1\text{ mA}$ , find the value of the midband gain.
  - (e) Select values for  $C_E$  and  $C_C$  to place the two break frequencies a decade apart and to obtain a lower 3-dB frequency of 100 Hz while minimizing the total capacitance.

3. Consider the circuit in Fig. P3 for the case:  $I = 200\text{ }\mu\text{A}$  and  $V_{OV} = 0.25\text{ V}$ ,  $R_{sig} = 200\text{ k}\Omega$ ,  $R_D = 50\text{ k}\Omega$ ,  $C_{gs} = C_{gd} = 1\text{ pF}$ . (18%)
  - (a) Find the dc gain.
  - (b) Find the high-frequency poles.
  - (c) Estimate the value of  $f_H$ .

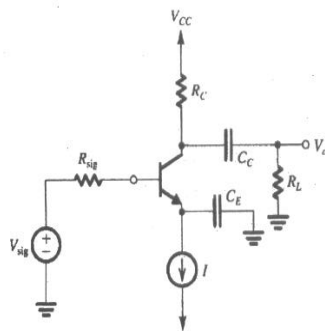


Fig. P2

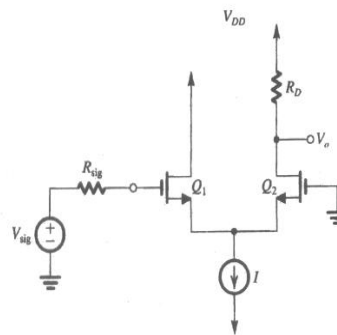


Fig. P3

國立中正大學九十四學年度碩士班招生考試試題  
系所別：光機電整合工程研究所 科目：電子學

第 2 節

第 2 頁，共 3 頁

4. For a shunt-shunt amplifier circuit shown below, the operational amplifier has open loop gain  $\mu = 10^3 V/V$ , input resistance  $R_{id} = 200K\Omega$ , common-mode input resistance  $R_{icm} = \infty$ , and output resistance  $r_o = 10K\Omega$ . Use the feedback method to find: (20%)
- the feedback factor  $\beta$
  - the closed loop gain of the feedback amplifier
  - the voltage gain  $V_o/V_s$
  - the input resistance  $R'_{if}$
  - the output resistance  $R'_{of}$

5. Consider the circuit as shown below, where both diodes have the same junction area as the output transistors. At  $20^\circ C$  the quiescent current is 5 mA and  $|V_{BE}| = 0.6V$ . Through a manufacturing error, the thermal coupling between the output transistors and the biasing diode-connected transistors is removed. After some output activity, the output devices heat up to  $60^\circ C$  while the biasing devices remain at  $20^\circ C$ . Thus while the  $V_{BE}$  of each device remains unchanged, the quiescent current in the output devices increases. To calculate the new current value, there are two effects to consider:  $I_s$  increases by about  $10\%/^\circ C$ , and  $V_T = KT/q$  since  $T = (273^\circ + \text{temperature in } ^\circ C)$  where  $V_T = 25mV$  only at  $20^\circ C$ . Assume  $\beta_N$  remains constant. (10%)
- What is the new values of  $I_Q$ ?
  - If the power supply is  $\pm 10V$ , what additional power is dissipated?

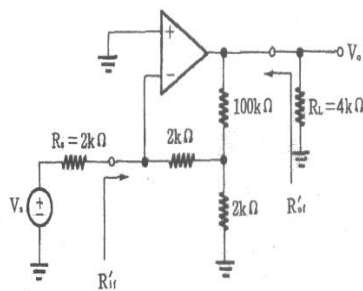


Fig. P4

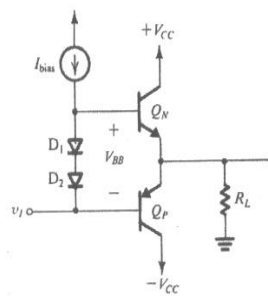


Fig. P5

國立中正大學九十四學年度碩士班招生考試試題

系所別：光機電整合工程研究所

科目：電子學

第 2 節

第 3 頁，共 3 頁

6. Consider the circuit as shown below, where the operational amplifier is assumed to be ideal,  $Q$  is the pole quality factor, and  $CR = 2Q/\omega_0$ . (20%)
- (a) Analyze the circuit to find out its transfer function  $V_o/V_s$ .
- (b) Find the voltage-driver ratio  $R_2/(R_1 + R_2)$  so that the circuit realizes an all-pass function.
- (c) Find the voltage-driver ratio  $R_2/(R_1 + R_2)$  so that the circuit realizes a notch function.

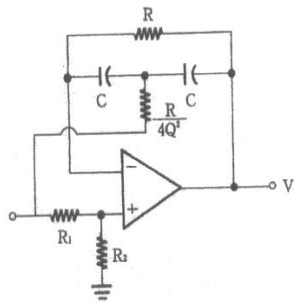


Fig. P6

The following numbers may be useful for your computation:

$e^1 \approx 2.71828$	$1.1^{25} \approx 10.83$
$e^{11} \approx 5.99 \times 10^4$	$1.1^{40} \approx 45.26$
$e^{24} \approx 2.65 \times 10^{10}$	$1.4^{30} \approx 24201.43$
$e^{37} \approx 1.17 \times 10^{16}$	$1.4^{15} \approx 155.57$
$e^{21.12} \approx 1.49 \times 10^9$	
$e^{21.33} \approx 1.83 \times 10^9$	
$e^{13.34} \approx 6.22 \times 10^5$	
$e^{13.55} \approx 7.67 \times 10^5$	