

- Use the Miller approximation to calculate the -3 dB frequency of the small-signal voltage gain of a differential stage as shown in Fig. P1, using these parameters: $W = 100 \mu\text{m}$, $L_{\text{drawn}} = 2 \mu\text{m}$, $L_d = 0.2 \mu\text{m}$, $k' = 60 \mu\text{A/V}^2$, $R_S = 10 \text{k}\Omega$, $R_L = 5 \text{k}\Omega$, $I_1 = 1 \text{mA}$, and $f_T = 3 \text{GHz}$ (at $I_D = 500 \mu\text{A}$). Note that L_{drawn} is the channel length drawn in the layout, and L_d is the lateral diffusion length. (10%)

 


Fig. P1

- Calculate the non-dominant pole magnitude for the circuit in (a). (5%)

- Derive the output impedance R_{out} of the circuit shown in Fig. P2. Assume that all transistors have small-signal output resistance r_o and operate in saturation with transconductance g_m . (15%)

 


Fig. P2

- The amplifier with feedback is shown in Fig. P3.
 - What is the feedback topology in this circuit? (3%)
 - Find the feedback factor. (4%)
 - Find the open-loop gain. (4%)
 - Find the closed-loop gain. (4%)
 - Find the closed-loop output impedance (5%)

 


Fig. P3

4. In the circuits of Fig. P4(a) and Fig. P4(b), assume that the reverse saturation current is 5×10^{-16} A for each diode and the thermal voltage is 25 mV.

- (a) In the circuit of Fig. P4(a), please calculate the current flowing through each diode. (5%)
 (b) In the circuit of Fig. P4(b), please calculate the current flowing through the resistor. (8%)
 (c) In the circuit of Fig. P4(c), please plot the input/output characteristic, assuming a 0.7-V constant-voltage drop model. (5%)

 


Fig. P4

5. The circuits in Fig. P5 is fabricated with the following process parameters: $\mu_n C_{ox} = 200 \mu A/V^2$, $\mu_p C_{ox} = 100 \mu A/V^2$, $V_{tn} = |V_{tp}| = 0.4$ V, and $\lambda = 0$ V⁻¹.
 (a) Please show that the drain current equals to $\mu_n C_{ox} \cdot \left(\frac{W}{L}\right) \cdot \left((V_{GS} - V_{tn}) \cdot V_{DS} - \frac{1}{2} V_{DS}^2\right)$ for N-type MOSFET to operate in triode region. (5%)
 (b) In the circuit shown in Fig. P5(a), compute W/L of Q₁ such that Q₁ can operate at the edge of saturation. Assume that the supply voltage V_{DD} is 1.8 V. (5%)
 (c) To provide a voltage gain of 200 for the MOS cascode circuit of Fig. P5(b) with a bias current of 1 mA, please determine the transistor size of $(W/L)_{Q1} = (W/L)_{Q2}$. Assume that $\lambda = 0.1$ V⁻¹ in this case. (10%)

 


Fig. P5

6. (a) A CMOS logic gate is required to provide the function of $Y = (A + B) \cdot C + D \cdot (E \cdot F + G)$, please sketch the schematic using MOS transistors. (4%)
 (b) Please provide suitable transistor sizes for the circuit of (a) to have equal rise and fall times. Assume that $\mu_n = 2\mu_p$. (4%)
 (c) Please use a CMOS logic inverter to derive the dynamic power dissipation. Assume that the supply voltage, operating frequency, output load capacitance are V_{DD}, f, and C_L. (4%)